

3-1 Given the sinusoid $10 \sin(10\pi t - 45^\circ)$, calculate its amplitude, rms value, angular frequency, period, frequency and phase angle.

3-2 Find the phase angle between $u_1(t) = 200\sqrt{2} \sin(5t + 30^\circ)$ and $u_2(t) = 50 \cos(5t)$. Does u_1 leads or lags u_2 ?

3-3 Find the phase angle between $i_1(t) = -4 \sin(417t + 30^\circ)$ and $i_2(t) = -7 \cos(417t - 35^\circ)$. Does i_1 leads or lags i_2 ?

3-4 Given $i_1(t) = 2\sqrt{2} \sin(\omega t + 45^\circ) \text{ A}$ and $i_2(t) = 2\sqrt{2} \cos(\omega t - 45^\circ) \text{ A}$, find their sum $i(t) = i_1(t) + i_2(t)$.

3-5 Given $u_1(t) = 20\sqrt{2} \sin(\omega t + 45^\circ) \text{ V}$ and $u_2(t) = -10\sqrt{2} \cos(\omega t - 30^\circ) \text{ V}$, find their sum $u(t) = u_1(t) + u_2(t)$.

3-6 Find the sinusoids corresponding to these phasors: a) $\underline{U} = -10 e^{j30^\circ} \text{ V}$; b) $\underline{I} = 2\sqrt{2}(\cos 45^\circ - j \sin 45^\circ) \text{ A}$; c) $\underline{I} = j(5 - j12) \text{ A}$.

3-7 Using the phasor approach, determine the current $i(t)$ in a circuit described by the integrodifferential equation


$$4i(t) + 8 \int i(t)dt - 3 \frac{di(t)}{dt} = 50\sqrt{2} \sin(2t + 75^\circ).$$

3-8 Find the voltage $u(t)$ in a circuit described by the integrodifferential equation

$$2\sqrt{2} \frac{du(t)}{dt} + 5\sqrt{2} u(t) + 10\sqrt{2} \int u(t)dt = 50\sqrt{2} \sin(5t - 30^\circ)$$


using the phasor approach.

3-9 Find the circuit current, $i(t)$, and capacitor-voltage, $u_C(t)$, for the circuit below.

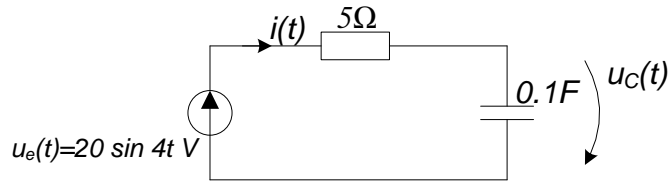

Problem 3-9


3-10 The circuit parameters for the RLC series circuit below are $R=20\Omega$, $L=40\text{mH}$, $C=50\mu\text{F}$, and the supplying voltage: $u(t) = 200 \sin(1000t - 30^\circ) \text{ V}$. Calculate: a) the inductive and capacitive reactances and the circuit impedance, X_L , X_C , Z ; b) the rms and the instantaneous value of the current, I , $i(t)$; c) the rms and the instantaneous value of resistance-voltage, U_R , $u_R(t)$; d) the rms and the instantaneous value of inductance-voltage, U_L , $u_L(t)$; e) the rms and the instantaneous value of capacitance-voltage, U_C , $u_C(t)$. Draw the circuit diagram.

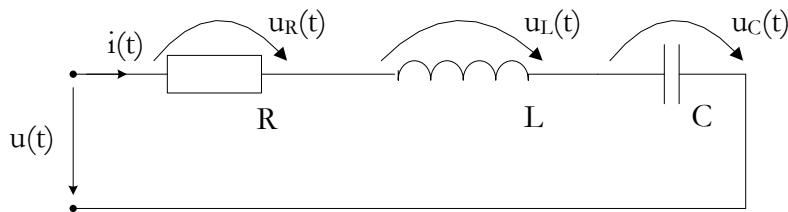

Problem 3-14


3-11 For an RLC series circuit we know $R=30\Omega$, $X_L = \omega L = 80\Omega$, $X_C = \frac{1}{\omega C} 40\Omega$ and the supplying voltage $u(t) = 100 \sqrt{2} \sin(100\pi t - 60^\circ) \text{ V}$. Calculate: a) the impedance in phasor form and the circuit impedance, \underline{Z} , Z ; b) the rms and the instantaneous value of circuit current, I , $i(t)$; c) the active, reactive and apparent power, P , Q , S . Verify the conservation of the active and the reactive power. Draw the circuit diagram.

3-12 For the circuit below we know $R=10\Omega$, $X_L = \omega L = 5\Omega$, $X_C = \frac{1}{\omega C} = 15\Omega$ and the voltage $u_1(t) = 100 \sqrt{2} \sin 100\pi t \text{ V}$. Find the output voltage, $u_2(t)$.

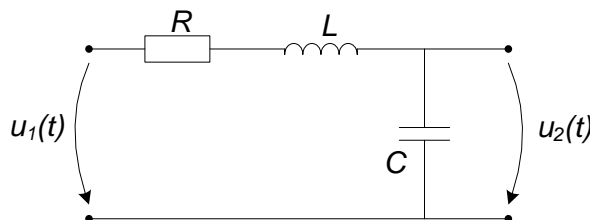


Problem 3-16

- 3-13** For the circuit below we know $\underline{Z}_1 = 3 + j4$, $\underline{Z}_2 = -j6$, $\underline{Z}_3 = 6 + j8$ and the rms current $I = 2\text{A}$. Find: a) the rms voltage on each impedance, U_1 , U_2 , U_3 ; the rms value of the supplying voltage, $u(t)$; c) the active, reactive and apparent power, P , Q , S .

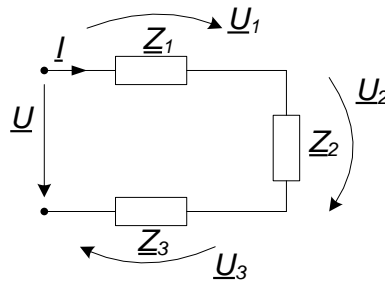


Problem 3-17

- 3-14** For the circuit below we know $R=10\Omega$, $L = \frac{3}{10\pi}\text{H}$, $C = \frac{1}{2.1\pi}\text{mF}$, and the supplying voltage: $u_e(t) = 100\sqrt{2}\sin(100\pi t - 60^\circ)\text{V}$. Calculate: a) the equivalent impedance and the circuit impedance regarding the source terminals, \underline{Z} , Z ; b) the rms value of the current, I ; c) the instantaneous value of the inductor-voltage, $u_L(t)$; d) the active, reactive and apparent power, P , Q , S . Verify the active and reactive power conservation.

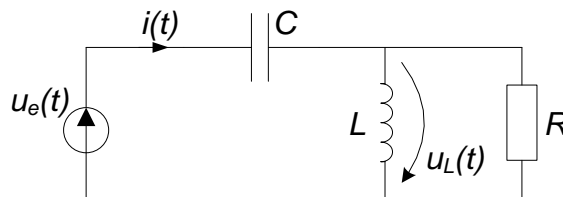


Problem 3-18

- 3-15** For the circuit below we know $R = 15\Omega$, $X_L = \omega L = 30\Omega$, $X_M = \omega M = 20\Omega$, $X_C = \frac{1}{\omega C} = 50\Omega$, and supplying voltage $u(t) = 100\sqrt{2}\sin(100\pi t + 60^\circ)\text{V}$. Determine: a) the phasor form of the equivalent impedance and the circuit impedance, \underline{Z} , Z ; b) the rms and the instantaneous value of the current, I , $i(t)$; the rms and the instantaneous voltage indicated in figure, U_L , $u_L(t)$.

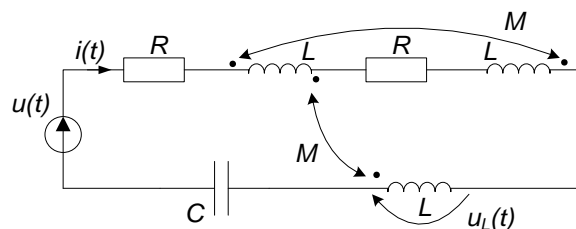


Problem 3-20

- 3-16** Determine the instantaneous value of current, $i_1(t)$, and the rms output-voltage U_2 for the circuit below. The circuit parameters are: $R = 40\Omega$, $X_{L1} = X_{L2} = 60\Omega$, $X_M = 30\Omega$, $X_C = 20\Omega$ and the supplying voltage $u_1(t) = 400\sin(500t - 30^\circ)\text{V}$.

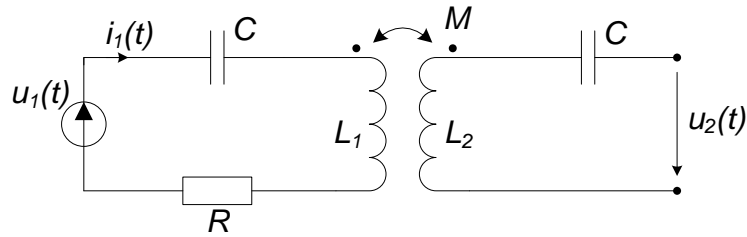


Problem 3-22

3-17 The voltage and the current absorbed by the sub-circuit below are: $u(t) = 200\sqrt{2}\sin(500t - 30^\circ)$ V and $i(t) = 5\sin(500t + 60^\circ)$ A. Write the voltage and current phasor operator, \underline{U} , \underline{I} . Find the impedance phasor operator, \underline{Z} , the circuit impedance, Z , the active power, P , and the reactive power, Q , removed by the sub-circuit.

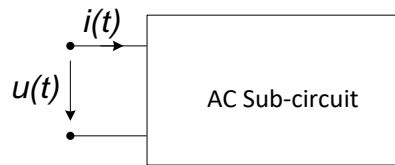


Problem 3-25

3-18 For the circuit below find the equivalent impedance \underline{Z}_e regarding terminals a and b. The circuit parameters are $R_1 = R_2 = R_3 = 10\Omega$, $L_3 = \frac{20}{\pi}$ mH, $C_2 = \frac{5}{\pi}$ mF, and $f = 50$ Hz.

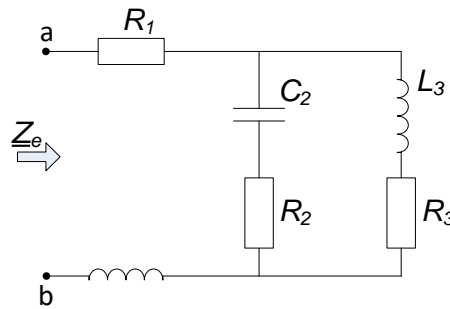


Problem 3-30

3-19 For the circuit below find the equivalent impedance \underline{Z}_e regarding terminals a and b. The circuit parameters are $R=10\Omega$, $L = \frac{100}{\pi}$ mH, $C = \frac{1}{\pi}$ mF, and $f = 50$ Hz.

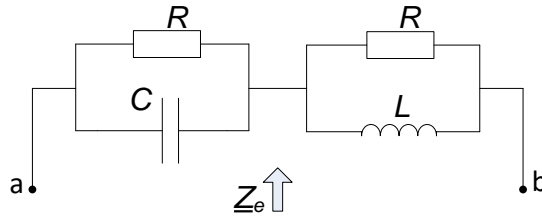


Problem 3-31

3-20 For the circuit below we know $\underline{Z}_1 = 10 + j40$, $\underline{Z}_2 = 20 - j20$, $\underline{Z}_3 = 20 + j20$ and rms current $I = 4\text{A}$. Find: a) the equivalent impedance regarding the source terminals; b) the rms and instantaneous value of supplying voltage, U_e , $u_e(t)$; the active, reactive and apparent power, P , Q , S .

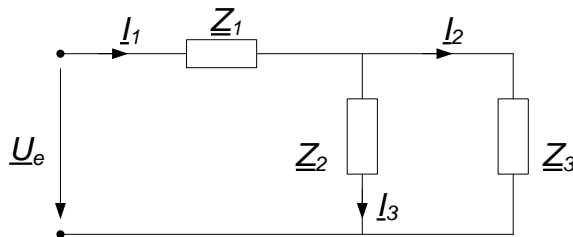


Problem 3-33

3-21 For the circuit below find the potentials of the circuit nodes. Calculate the circuit currents.

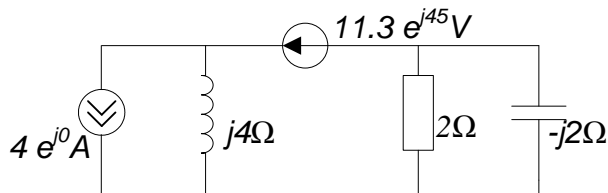


Problem 3-37

3-22 For the circuit below find the potentials of the circuit nodes. Calculate the circuit currents.

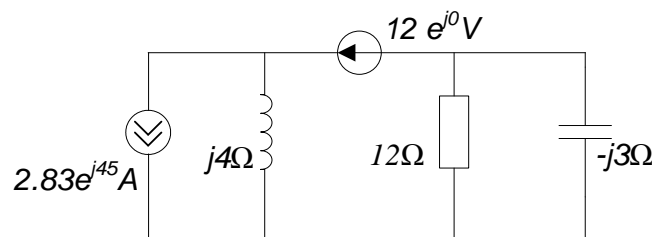


Problem 3-39

3-23 For the circuit below determine the impedance value \underline{Z} which will absorb the greatest power from the circuit.

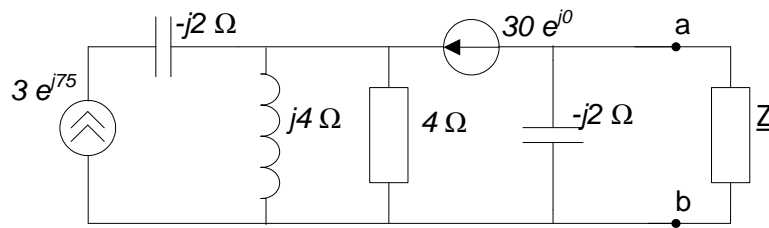

Problem 3-43

3-24 For the circuit below determine the impedance value \underline{Z} which will absorb the greatest power from the circuit.

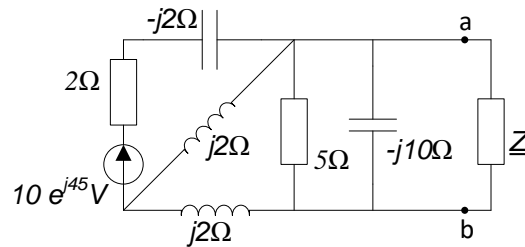

Problem 3-44