

# Logică digitală

-Curs 12-  
Memorii

# Outline

---

- ☐ Clasificare
  - ☐ Organizare memorii
  - ☐ Creștere bandwidth/spatiu de adrese
  - ☐ Ciclu de sciire
  - ☐ Ciclu de citire
  - ☐ Stivă și coada
-

# Clasificare memorii

Scriere și Citire		Non-volatile scriere și citire	ROM (numai citire)
Acces random	Acces Non-random	EPROM EEPROM FLASH	Măști programate
SRAM DRAM	FIFO LIFO		

- ❑ Din punct de vedere al modului de adresare:
  - ❑ prin ADRESĂ
  - ❑ prin CONȚINUT (ex. mem. Cache L1)

# Clasificare memorii

---

## □ Metrici:


- **Densitatea memoriei** (număr biți/ $\mu\text{m}^2$ ) și **capacitate**
  - **Timp de acces** (timpul necesar unei op. de scriere sau citire) și **throughput**
  - **Consumul de putere**
-

# Random Access Memory (RAM)

## Memorie cu acces aleator

MEMORY ADDRESS		MEMORY CONTENT
Binary	Decimal	
0...000	0	011...0100
0...001	1	011...0100
0...010	2	101...1100
0...011	3	101...0001
0...100	4	011...0101
0...101	5	010...0101
0...110	6	110...0011
0...111	7	101...0001
⋮	⋮	⋮
1...110	$2^n-2$	000...0010
1...111	$2^n-1$	111...0110

$\longleftrightarrow m \text{ bits}$

 


# Random Access Memory (RAM)

## Memorie cu acces aleator

---

- ☐ De câte linii de adrese avem nevoie pentru a accesa o memorie de 1kbit?
  - ☐ De câte linii de adrese avem nevoie pentru a accesa o memorie de 64kbit?
-

# RAM: organize

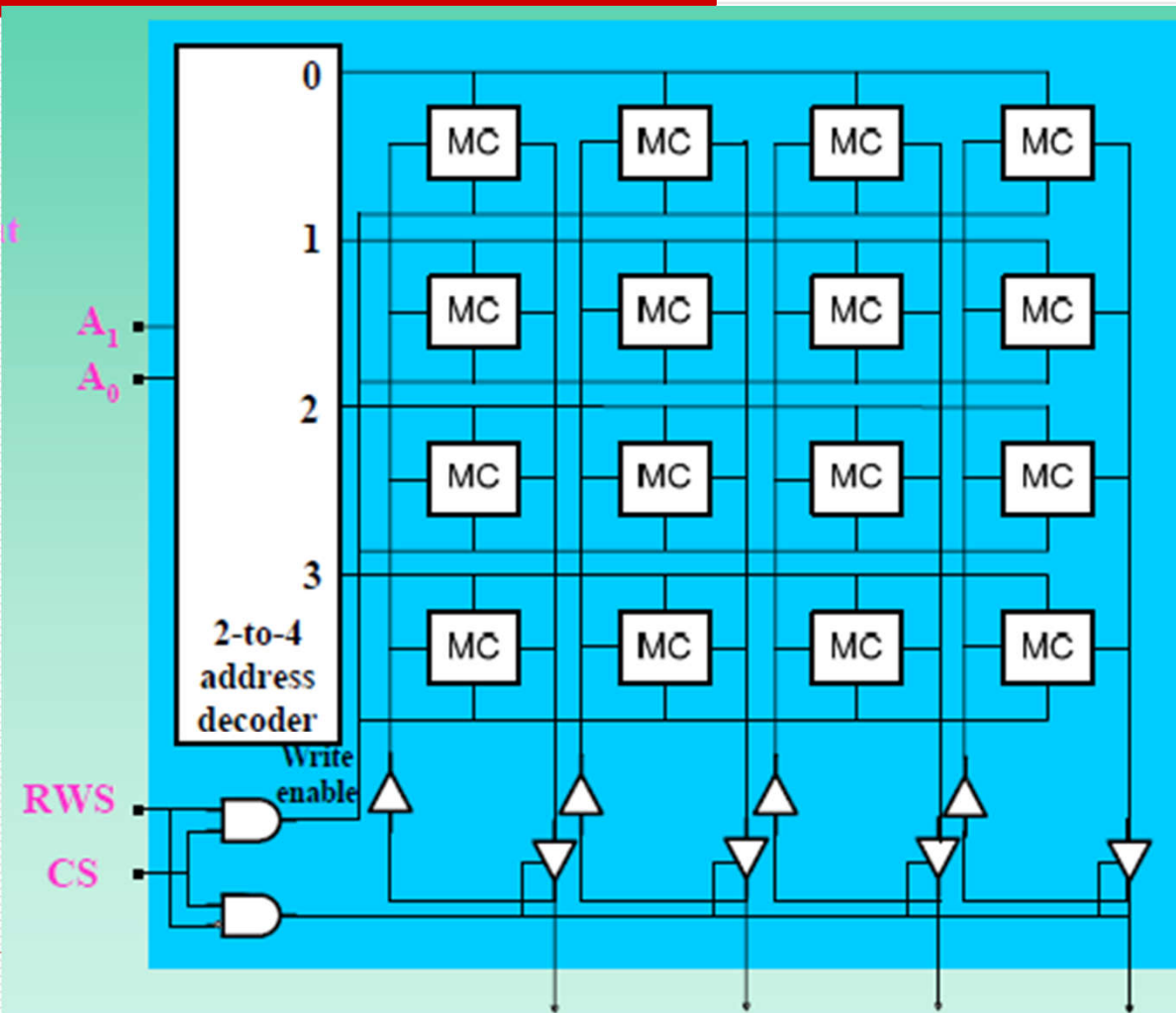


# SRAM vs DRAM

---


- ❑ SRAM memorează starea câtă vreme e alimentat. DRAM-ul are nevoie de alimentare + refresh (controler mai complex)
  - ❑ DRAM are densitate mai mare (1 tranzistor /celulă) în comparație cu SRAM-ul (4-6 pt. cross-cupled inverters), dar:
    - Are nevoie de ciclu refresh.
    - Citirea e distructivă, deci trebuie rescrisă informația imediat după
  - ❑ FPGA-urile folosesc tehnologie SRAM uzual
-




# Ciclu RAM de citire

 


# Ciclu RAM scriere

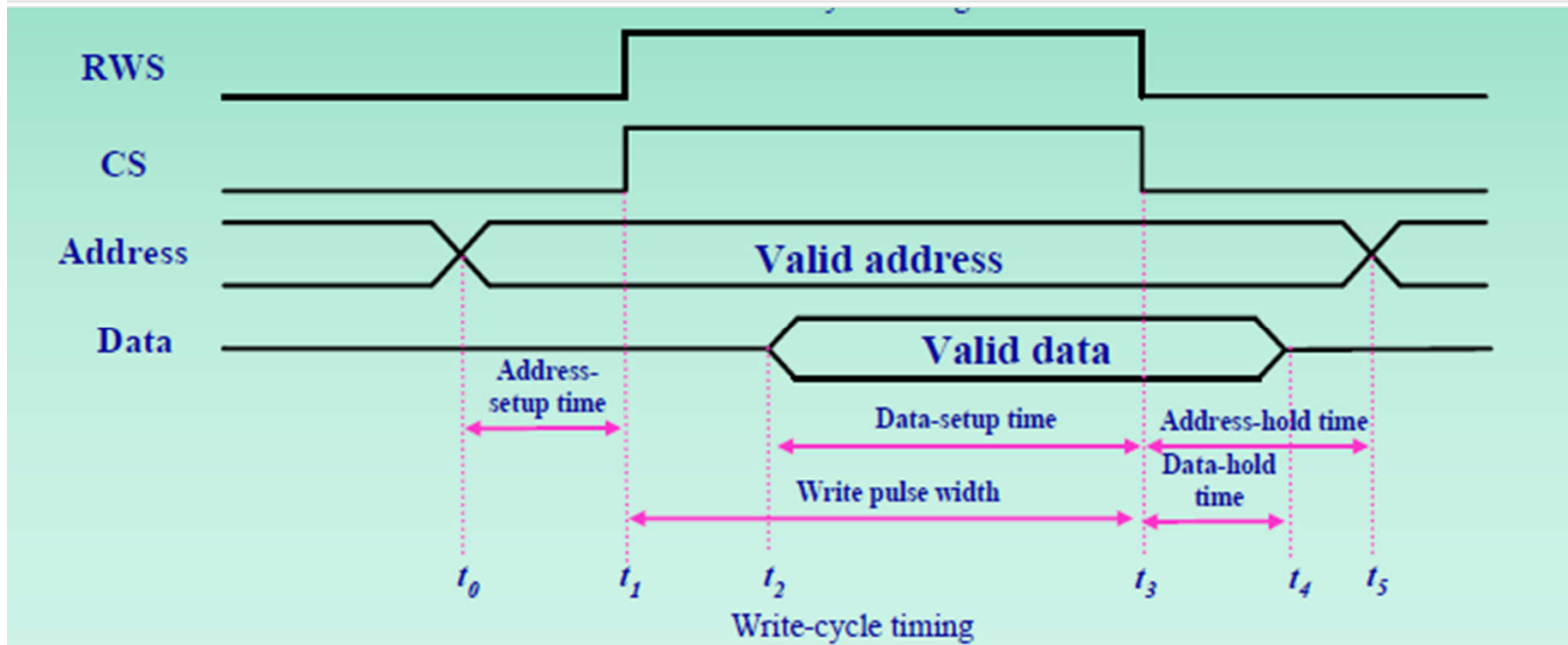


# 16K x 32 RAM design with 16K x 8 RAMs

 

# 64K x 8 RAM design with 16K x 8 RAMs

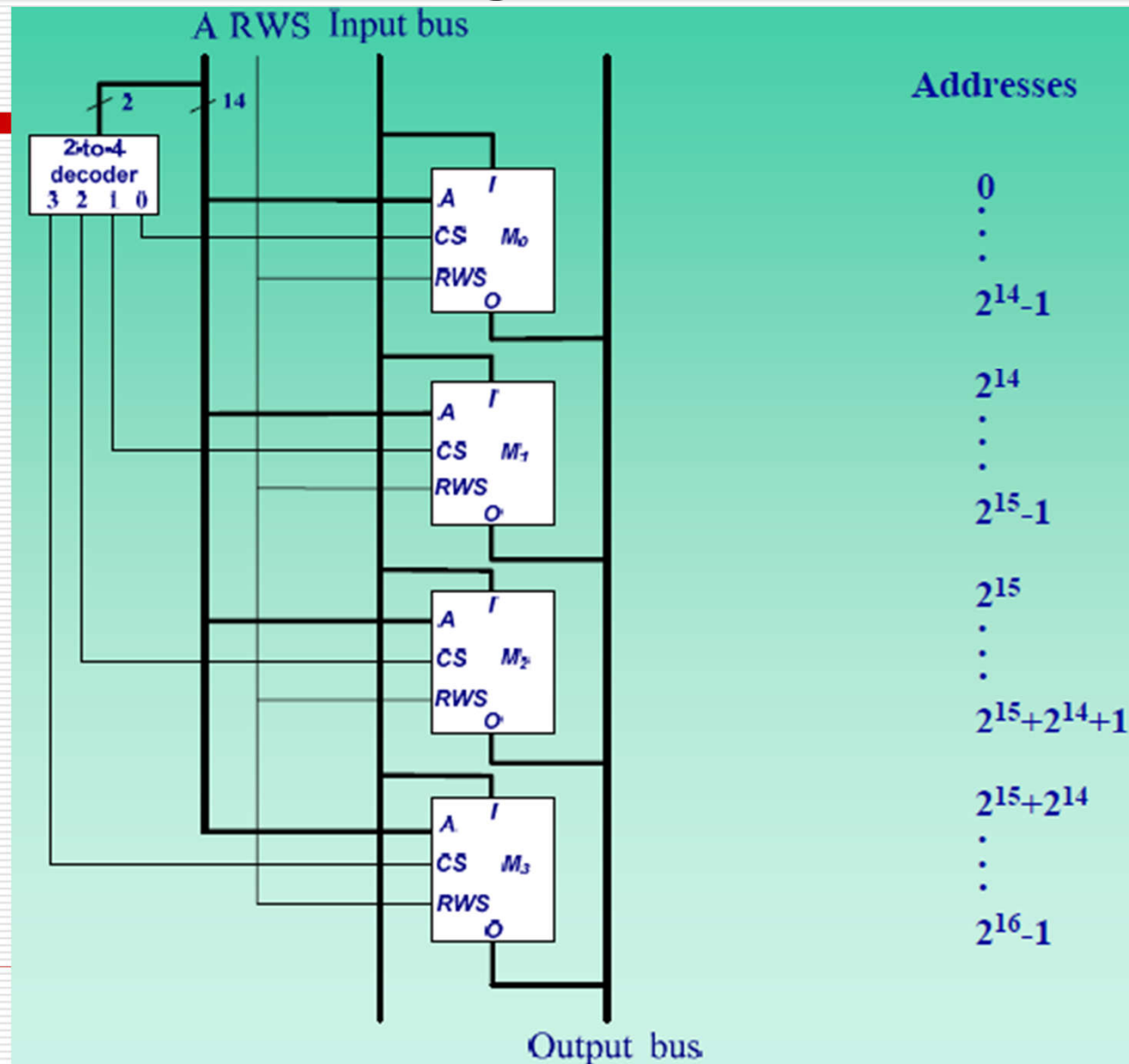

# Stiva

 

# Stiva

---

- ☐ 4 word, m bit push-down stack cu:
    - m input lines (IN),
    - m output lines (OUT),
  - ☐ semnale de control:
    - push/pop :
      - ☐ 0 data este adaugata in stiva,
      - ☐ 1 pentru scoaterea datei din stiva
    - Enable: permite operarea stivei
    - Semnale de stare (Empty si Full)
-

# Stiva 4 cuv.

Push/Pop	Enable	Operations
X	0	No change
0	1	Push
1	1	Pop

Operation table

Push/Pop Enable		Shift register controls		Counter controls	
		S <sub>1</sub>	S <sub>0</sub>	D	E
X	0	0	0	X	0
0	1	1	1	0	1
1	1	1	0	1	1

Control table

Counter outputs			Empty	Full
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>		
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1

Output table

## Registru deplasare

Present state		Operation	Next state			
S <sub>1</sub>	S <sub>0</sub>		Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	No change	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	1	Load input	I <sub>3</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>
1	0	Shift left	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	I <sub>R</sub>
1	1	Shift right	I <sub>L</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>


Operation table

## Numărător

Load	E	D	Operations
0	0	X	No change
0	1	0	Count up
0	1	1	Count down
1	X	X	Load the input


Operation table

# Stiva 4 cuv.

 



# Stiva – implementare fol. 1kB SRAM

 

Push/Pop	Enable	Operations
X	0	No change
0	1	Push
1	1	Pop

Operation table

		Selector control	Memory controls		Counter controls	
Push/Pop	Enable	S	CS	RWS	D	E
X	0	X	0	0	X	0
0	1	1	1	1	0	1
1	1	0	1	0	1	1


Control table

# Stiva – implementare fol. 1kB SRAM


---

- ❑ Push: Data loc . RAM (TOP);  
Increment Top, Top+1
  - ❑ Pop: Data loc. RAM (Top-1) Date;  
Decrement Top, Top-1
  - ❑ Stivă plină: Top=1023;
  - ❑ Stivă goală: Top=0;
  - ❑ Locația cu dresa 1023 nu e încărcată  
niciodată (11 1111 1111)
-

# Stiva – implementare fol. 1kB SRAM

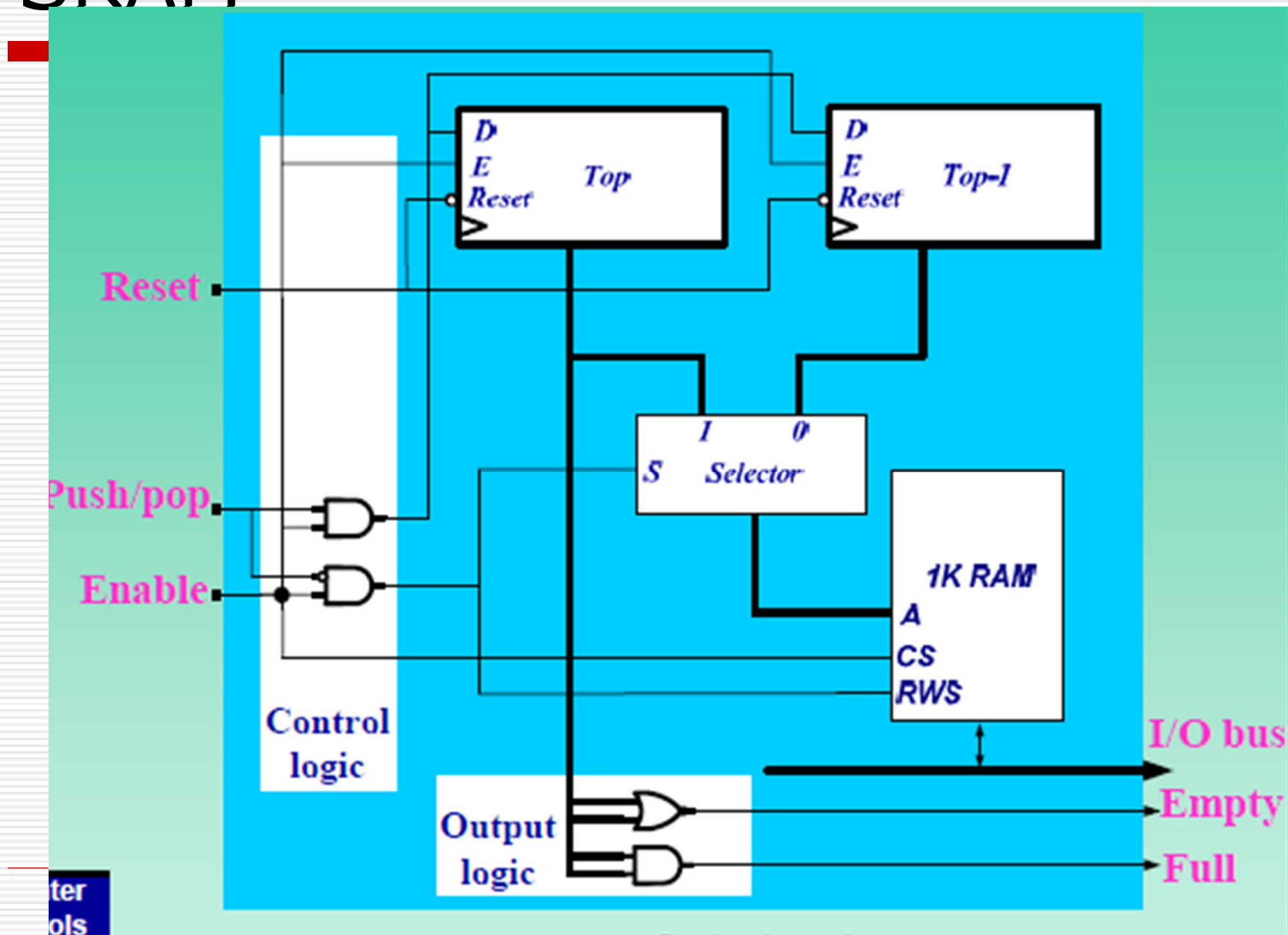

# FIFO

 

# FIFO – 4 cuvinte

READ/WRITE	ENABLE	OPERATIONS
X	0	No change
0	1	Read
1	1	Write

Operation table

READ/WRITE	ENABLE	$S_1$	$S_0$	$D$	$E$
X	0	0	0	X	0
0	1	0	0	1	1
1	1	1	0	0	1

Control table


# FIFO – 4 cuvinte

READ/WRITE ENABLE	OPERATIONS
X 0	No change
0 1	Read
1 1	Write


Operation table

READ/WRITE ENABLE	$S_1$	$S_0$	$D$	$E$
X 0	0	0	X	0
0 1	0	0	1	1
1 1	1	0	0	1

Control table

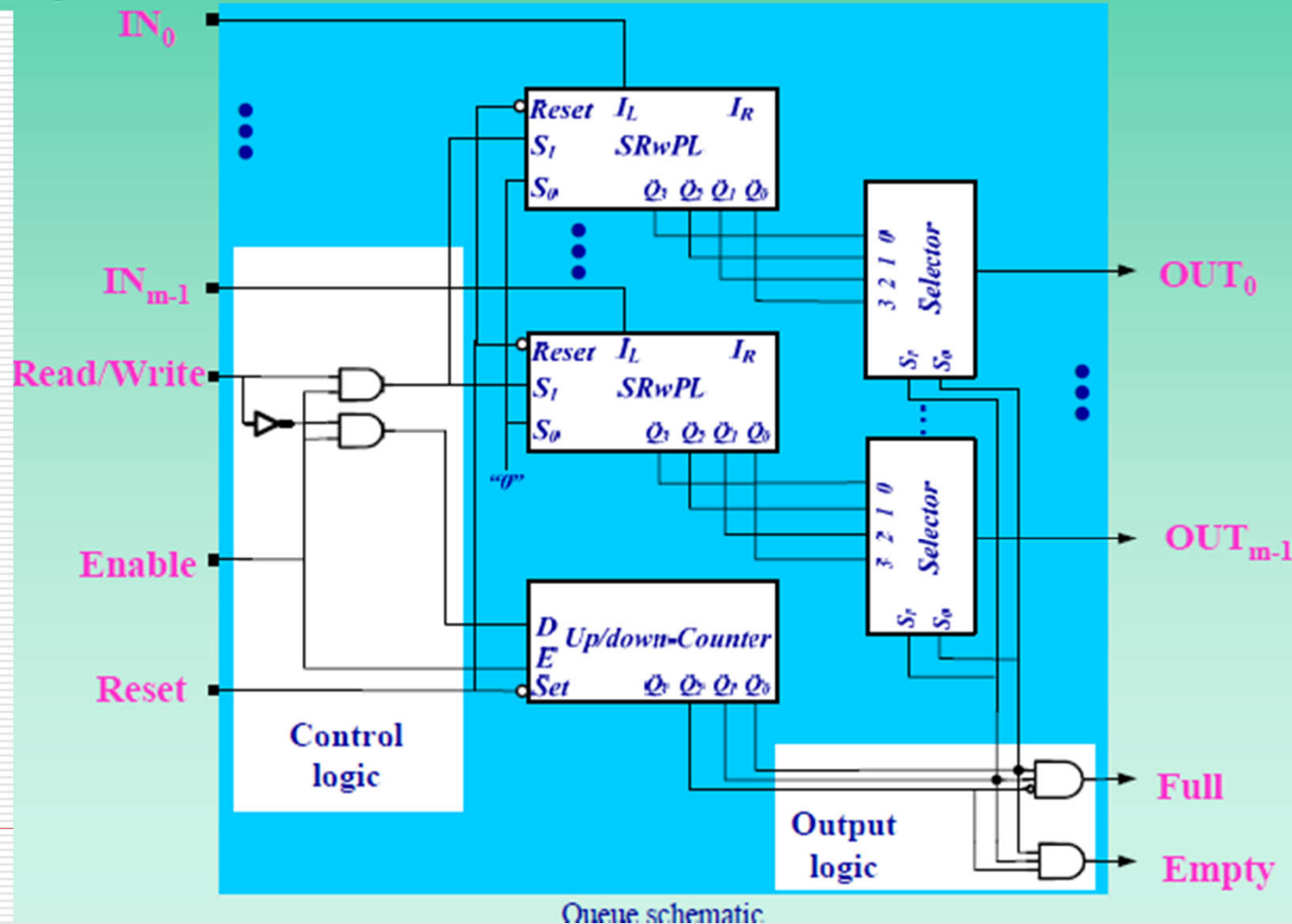

# FIFO - 1kB SRAM

 

Read/Write	Enable	Operations
X	0	No change
0	1	Read
1	1	Write

Operation table

Read/Write	Enable	S	CS	RWS	E (Front)	E (Back)
X	0	X	0	X	0	0
0	1	1	1	0	1	0
1	1	0	1	1	0	1

Control table




# FIFO - 1kB SRAM

<i>Read/Write</i>	<i>Enable</i>	<i>Operations</i>
<i>X</i>	<i>0</i>	<i>No change</i>
<i>0</i>	<i>1</i>	<i>Read</i>
<i>1</i>	<i>1</i>	<i>Write</i>

Operation table

<i>Read/Write</i>	<i>Enable</i>	<i>S</i>	<i>CS</i>	<i>RWS</i>	<i>E</i> <i>(Front)</i>	<i>E</i> <i>(Back)</i>
<i>X</i>	<i>0</i>	<i>X</i>	<i>0</i>	<i>X</i>	<i>0</i>	<i>0</i>
<i>0</i>	<i>1</i>	<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>	<i>0</i>
<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>

Control table

  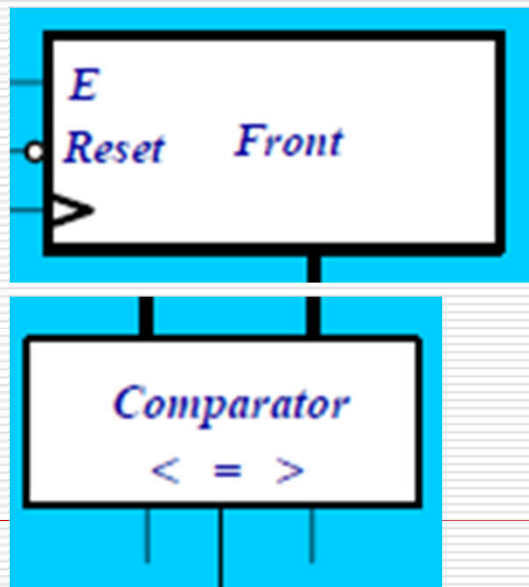




Read/Write	Enable	Operations
X	0	No change
0	1	Read
1	1	Write

Operation table

Read/Write	Enable	S	CS	RWS	E (Front)	E (Back)
X	0	X	0	X	0	0
0	1	1	1	0	1	0
1	1	0	1	1	0	1

Control table

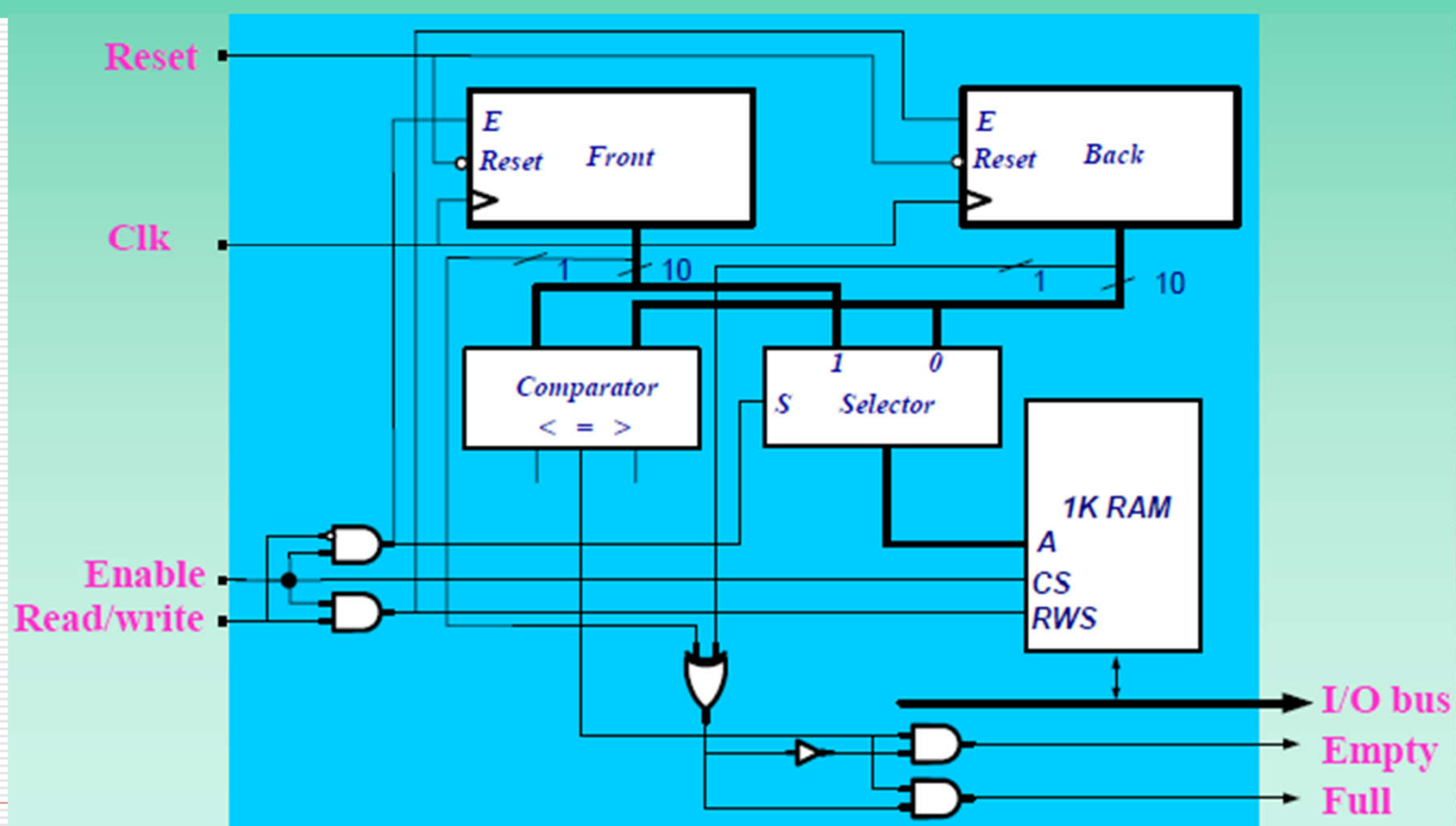

---

**Enough Talking Let's Get To It  
!!Brace Yourselves!!**

