

Logică digitală

-Curs 13-
Memorii

Outline

- ☐ Clasificare
 - ☐ Organizare memorii
 - ☐ Creștere latime de banda/spatiu de adrese
 - ☐ Ciclu de scriere
 - ☐ Ciclu de citire
 - ☐ Stivă și coada
-

Clasificare memorii

Scriere și Citire		Non-volatile scriere și citire	ROM (numai citire)
Acces random	Acces Non-random	EPROM EEPROM FLASH	Măști programate
SRAM DRAM	FIFO LIFO		

- ❑ Din punct de vedere al modului de adresare:
 - ❑ prin ADRESĂ
 - ❑ prin CONȚINUT (ex. mem. Cache L1)

Clasificare memorii

□ Metrici:


- **Densitatea memoriei** (număr biți/ μm^2) și **capacitate**
 - **Timp de acces** (timpul necesar unei op. de scriere sau citire) și **throughput**
 - **Consumul de putere**
-

Random Access Memory (RAM)

Memorie cu acces aleator

MEMORY ADDRESS		MEMORY CONTENT
Binary	Decimal	
0...000	0	011...0100
0...001	1	011...0100
0...010	2	101...1100
0...011	3	101...0001
0...100	4	011...0101
0...101	5	010...0101
0...110	6	110...0011
0...111	7	101...0001
⋮	⋮	⋮
1...110	2^n-2	000...0010
1...111	2^n-1	111...0110

$\longleftrightarrow m \text{ bits}$

 

Random Access Memory (RAM)

Memorie cu acces aleator


- ☐ De câte linii de adrese avem nevoie pentru a accesa o memorie de 1kbit?
 - ☐ De câte linii de adrese avem nevoie pentru a accesa o memorie de 64kbit?
-




SRAM vs DRAM

- ❑ SRAM memorează starea câtă vreme e alimentat. DRAM-ul are nevoie de alimentare + refresh (controler mai complex)
 - ❑ DRAM are densitate mai mare (1 tranzistor /celulă) în comparație cu SRAM-ul (4-6 pt. cross-cupled inverters), dar:
 - Are nevoie de ciclu refresh.
 - Citirea e distructivă, deci trebuie rescrisa informația imediat după
 - ❑ FPGA-urile folosesc tehnologie SRAM - BRAM
-


Ciclu RAM de citire

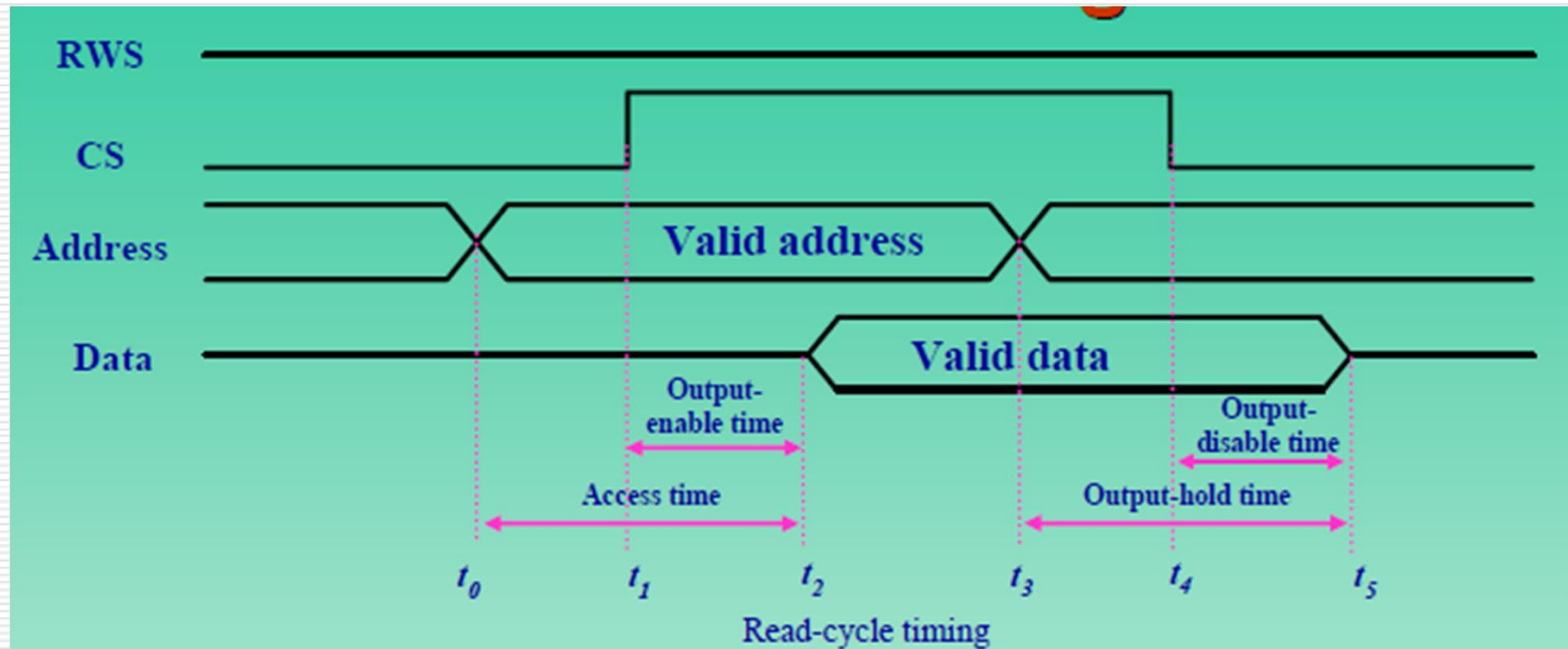


Ciclu RAM scriere

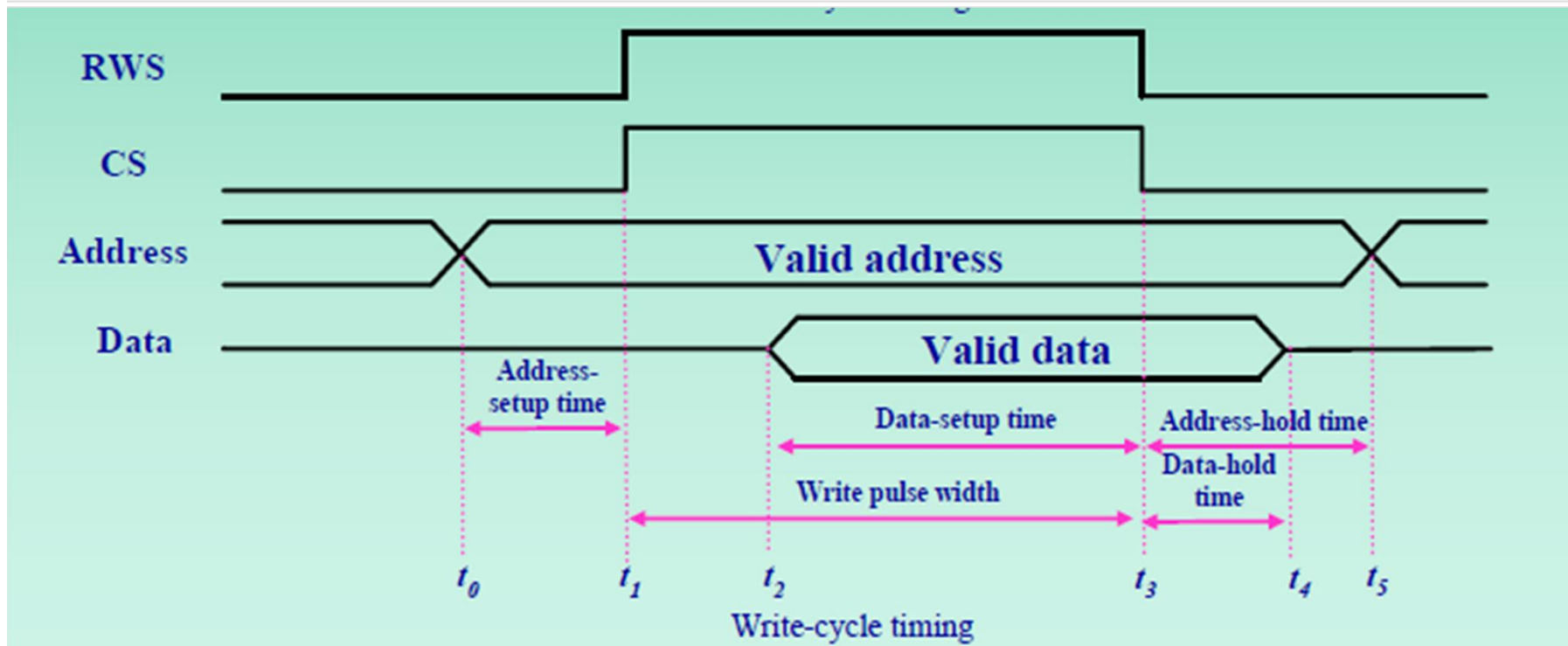


16K x 32 RAM design with 16K x 8 RAMs

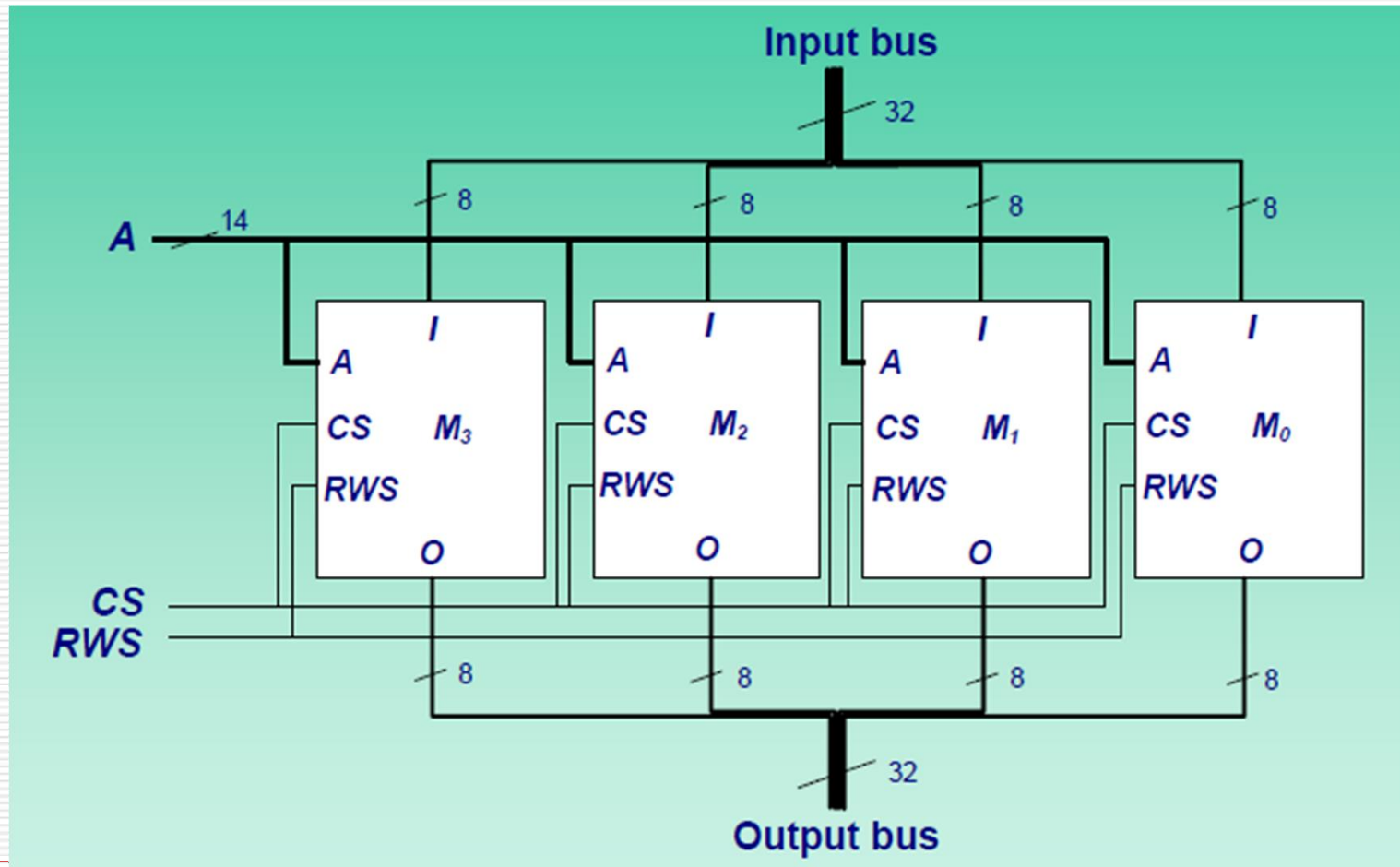

64K x 8 RAM design with 16K x 8 RAMs

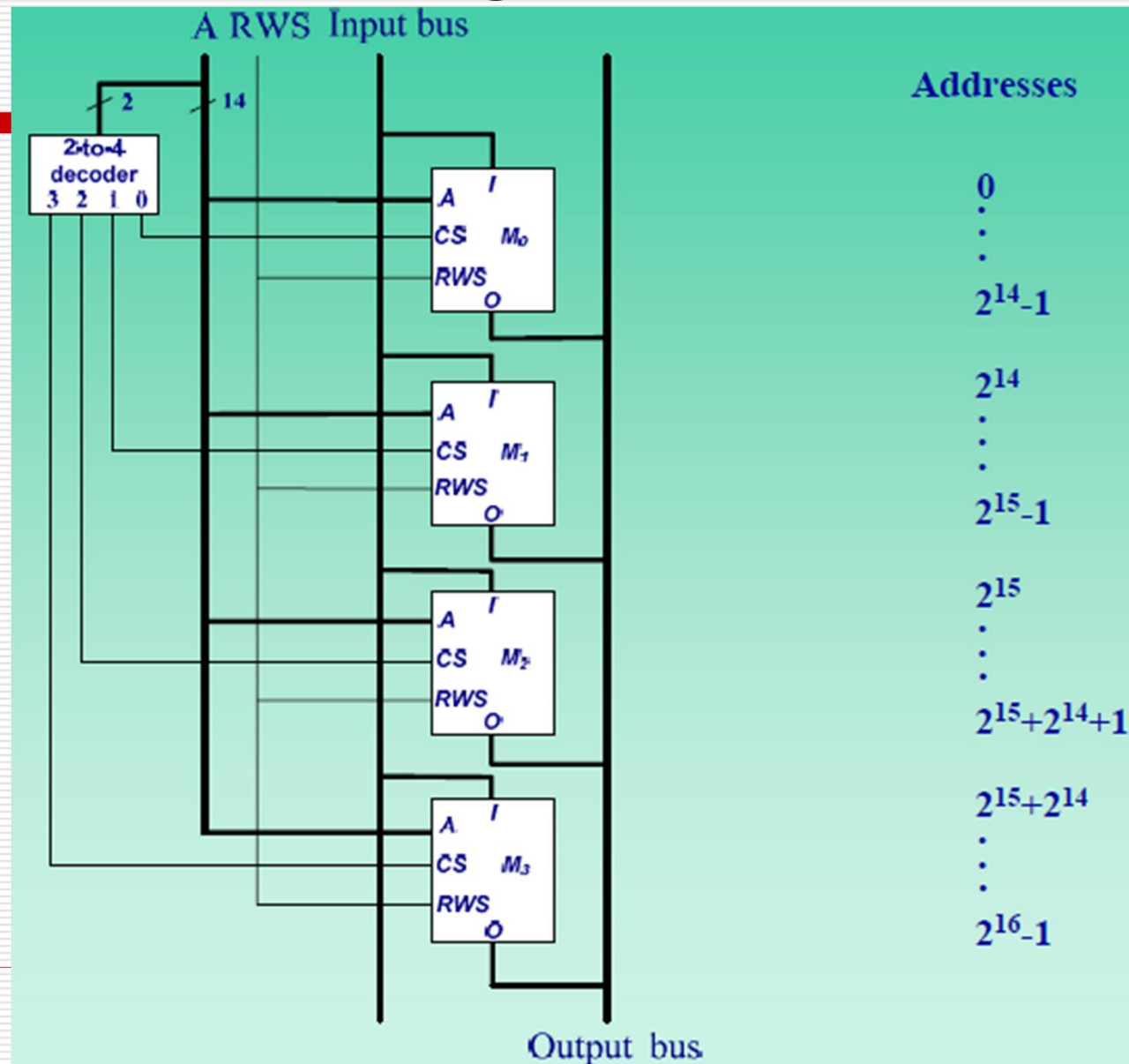

Stiva

 

Stiva

- ❑ 4 word, m bit push-down stack cu:
 - m input lines (IN),
 - m output lines (OUT),
 - ❑ semnale de control:
 - push/pop :
 - ❑ 0 data este adaugata in stiva,
 - ❑ 1 pentru scoaterea datei din stiva
 - Enable: permite operarea stivei
 - Semnale de stare (Empty si Full)
-

Stiva 4 cuv.

Push/Pop	Enable	Operations
X	0	No change
0	1	Push
1	1	Pop

Operation table

Push/Pop Enable		Shift register controls		Counter controls	
		S ₁	S ₀	D	E
X	0	0	0	X	0
0	1	1	1	0	1
1	1	1	0	1	1

Control table

Counter outputs			Empty	Full
Q ₂	Q ₁	Q ₀		
0	0	0	1	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1

Output table

Registru deplasare

Present state		Operation	Next state			
S ₁	S ₀		Q ₃	Q ₂	Q ₁	Q ₀
0	0	No change	Q ₃	Q ₂	Q ₁	Q ₀
0	1	Load input	I ₃	I ₂	I ₁	I ₀
1	0	Shift left	Q ₂	Q ₁	Q ₀	I _R
1	1	Shift right	I _L	Q ₃	Q ₂	Q ₁


Operation table

Numărător


Load	E	D	Operations
0	0	X	No change
0	1	0	Count up
0	1	1	Count down
1	X	X	Load the input

Operation table

Stiva 4 cuv.

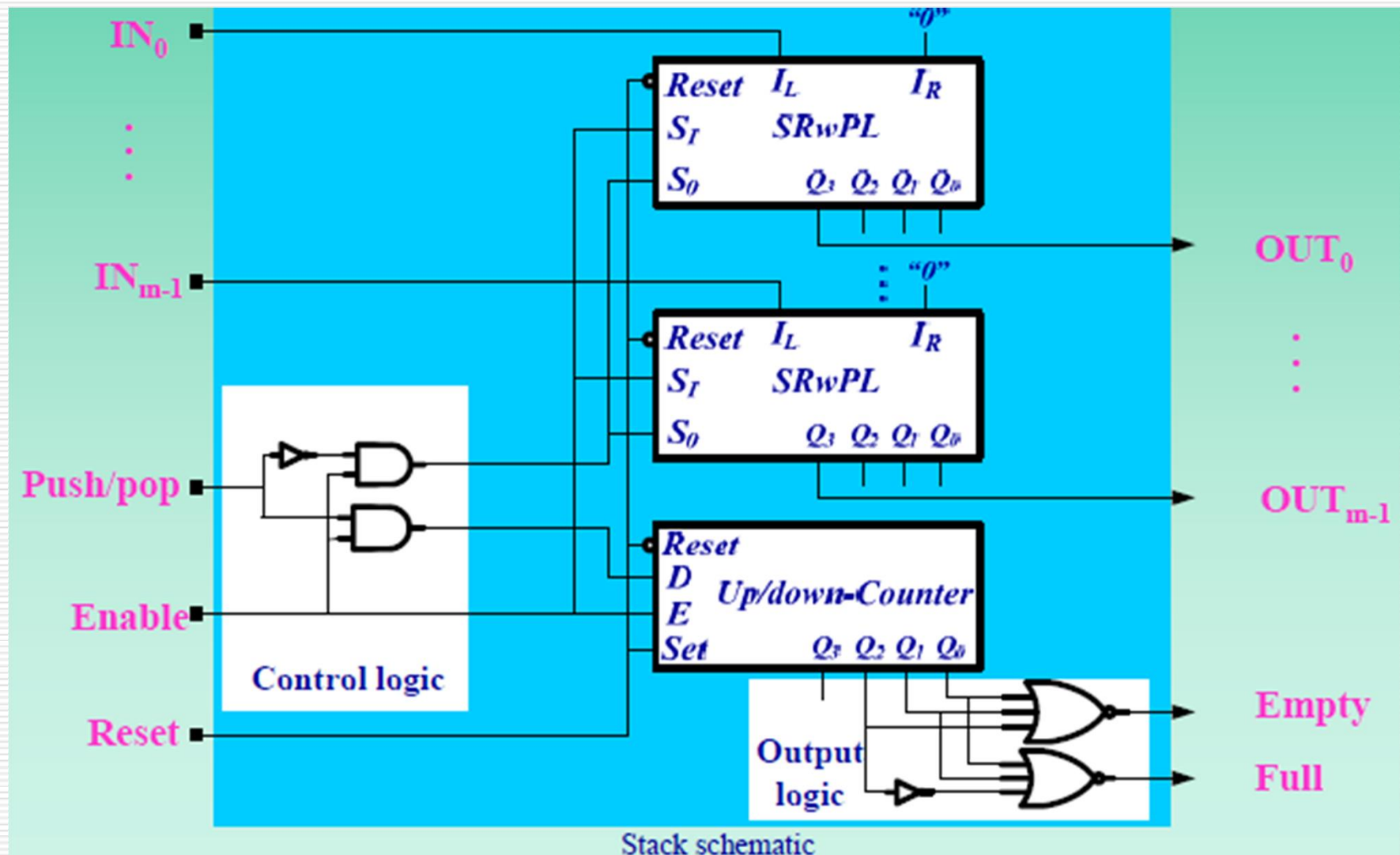

Stiva – implementare fol. 1kB SRAM

 

Push/Pop	Enable	Operations
X	0	No change
0	1	Push
1	1	Pop

Operation table


		Selector control	Memory controls		Counter controls	
Push/Pop	Enable	S	CS	RWS	D	E
X	0	X	0	0	X	0
0	1	1	1	1	0	1
1	1	0	1	0	1	1

Control table


Stiva – implementare fol. 1kB SRAM

- ❑ Push: Data loc . RAM (TOP);
Increment Top, Top-1
 - ❑ Pop: Data loc. RAM (Top-1) Date;
Decrement Top, Top-1
 - ❑ Stivă plină: Top=1023;
 - ❑ Stivă goală: Top=0;
 - ❑ Locația cu adresa 1023 nu e încărcată
niciodată (11 1111 1111)
-

Stiva – implementare fol. 1kB SRAM

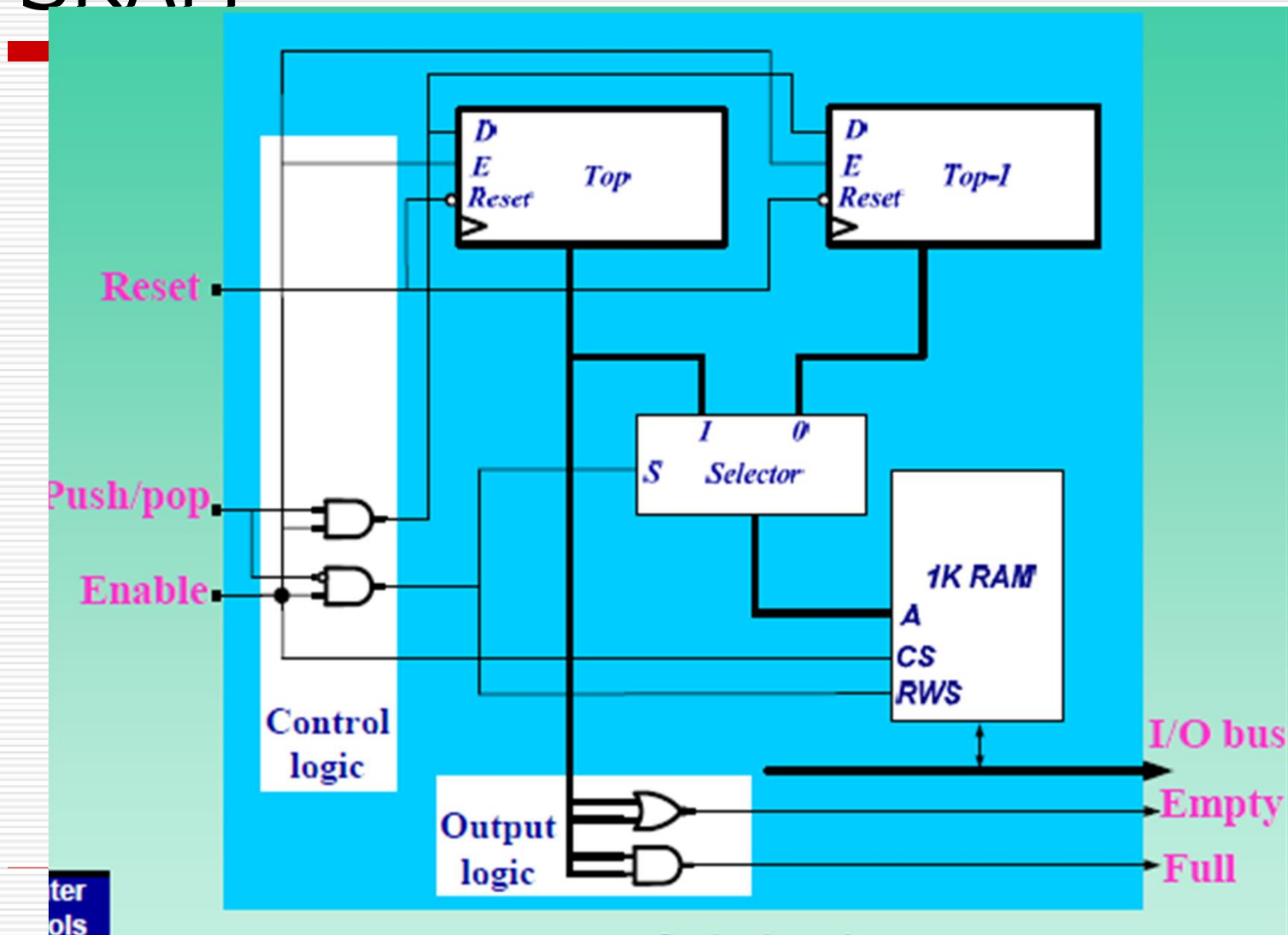

FIFO

 

FIFO – 4 cuvinte

READ/WRITE	ENABLE	OPERATIONS
X	0	No change
0	1	Read
1	1	Write

Operation table

READ/WRITE	ENABLE	S_1	S_0	D	E
X	0	0	0	X	0
0	1	0	0	1	1
1	1	1	0	0	1

Control table

Registru deplasare

Present state		Operation	Next state			
S_1	S_0		Q_3	Q_2	Q_1	Q_0
0	0	No change	Q_3	Q_2	Q_1	Q_0
0	1	Load input	I_3	I_2	I_1	I_0
1	0	Shift left	Q_2	Q_1	Q_0	I_R
1	1	Shift right	I_L	Q_3	Q_2	Q_1

Operation table


FIFO – 4 cuvinte

READ/WRITE ENABLE	OPERATIONS
X 0	No change
0 1	Read
1 1	Write

Operation table


READ/WRITE ENABLE	S_1	S_0	D	E
X 0	0	0	X	0
0 1	0	0	1	1
1 1	1	0	0	1

Control table

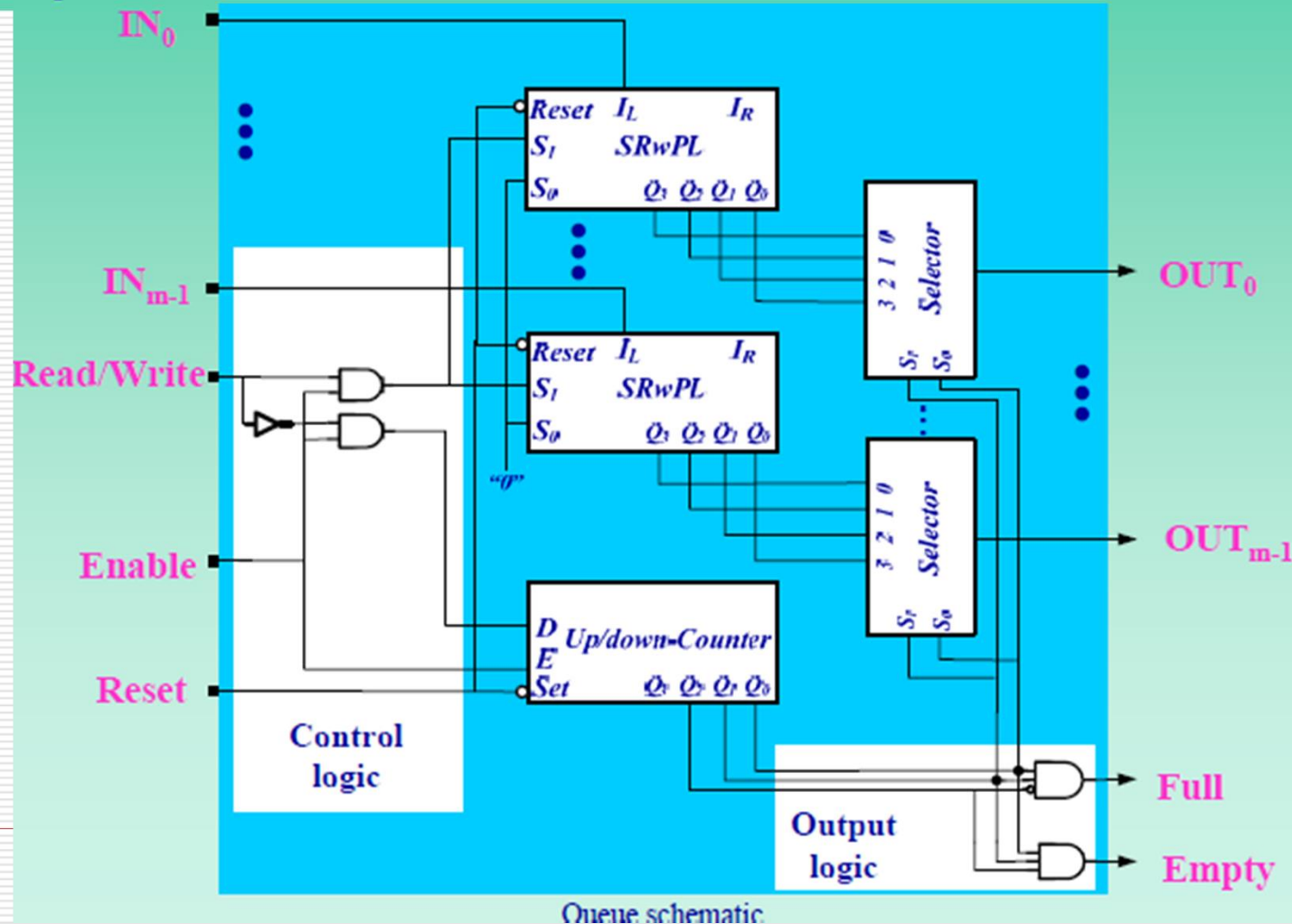

Queue schematic

FIFO - 1kB SRAM

 

Read/Write	Enable	Operations
X	0	No change
0	1	Read
1	1	Write

Operation table

Read/Write	Enable	S	CS	RWS	E (Front)	E (Back)
X	0	X	0	X	0	0
0	1	1	1	0	1	0
1	1	0	1	1	0	1

Control table



FIFO - 1kB SRAM

<i>Read/Write</i>	<i>Enable</i>	<i>Operations</i>
<i>X</i>	<i>0</i>	<i>No change</i>
<i>0</i>	<i>1</i>	<i>Read</i>
<i>1</i>	<i>1</i>	<i>Write</i>

Operation table

<i>Read/Write</i>	<i>Enable</i>	<i>S</i>	<i>CS</i>	<i>RWS</i>	<i>E</i> <i>(Front)</i>	<i>E</i> <i>(Back)</i>
<i>X</i>	<i>0</i>	<i>X</i>	<i>0</i>	<i>X</i>	<i>0</i>	<i>0</i>
<i>0</i>	<i>1</i>	<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>	<i>0</i>
<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>

Control table

 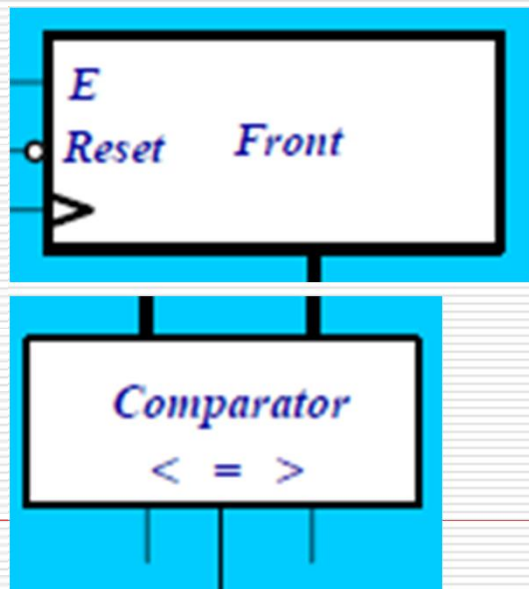


Read/Write	Enable	Operations
X	0	No change
0	1	Read
1	1	Write


Operation table

Read/Write	Enable	S	CS	RWS	E (Front)	E (Back)
X	0	X	0	X	0	0
0	1	1	1	0	1	0
1	1	0	1	1	0	1


Control table

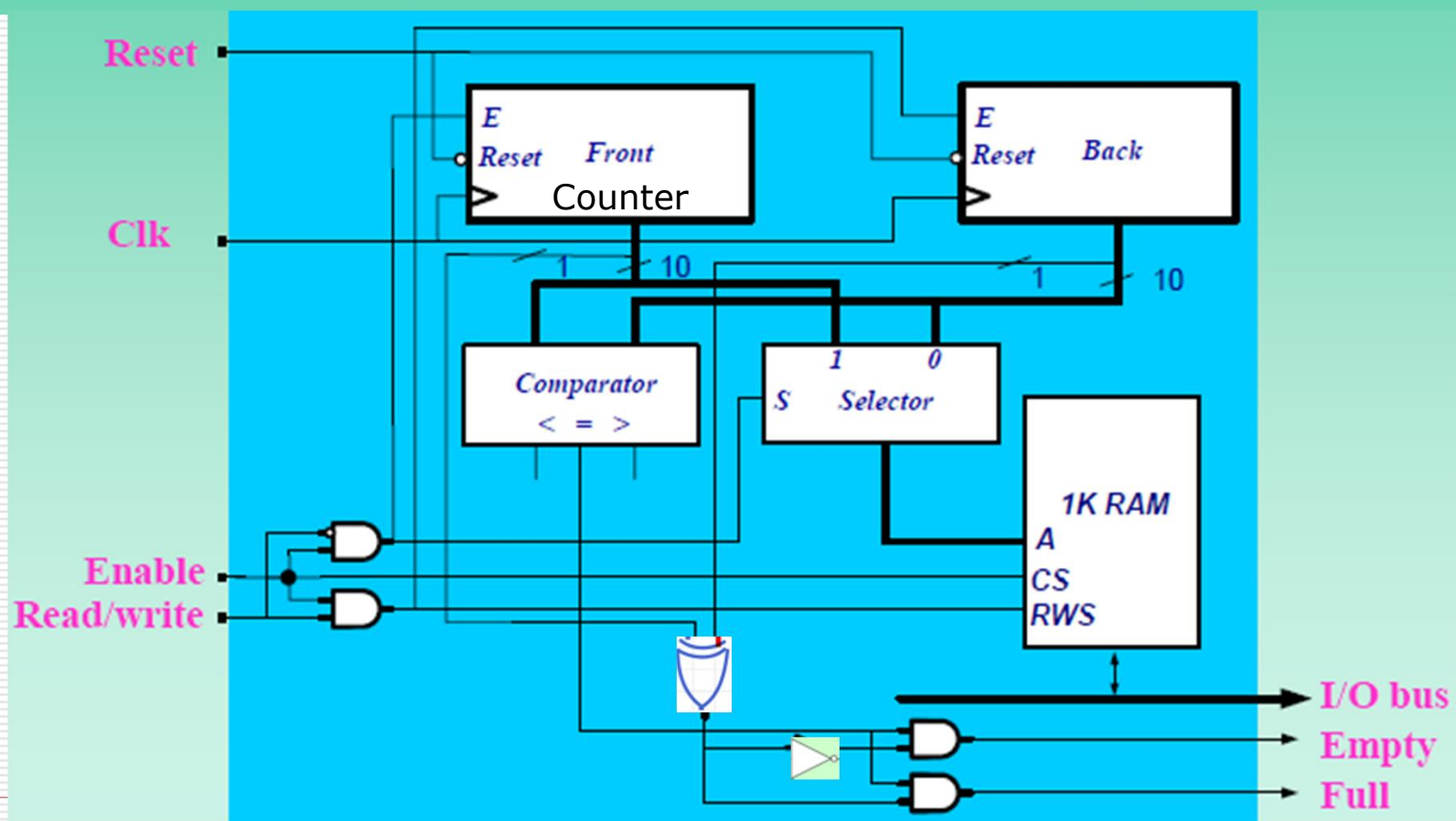

Debouncing – problem statement

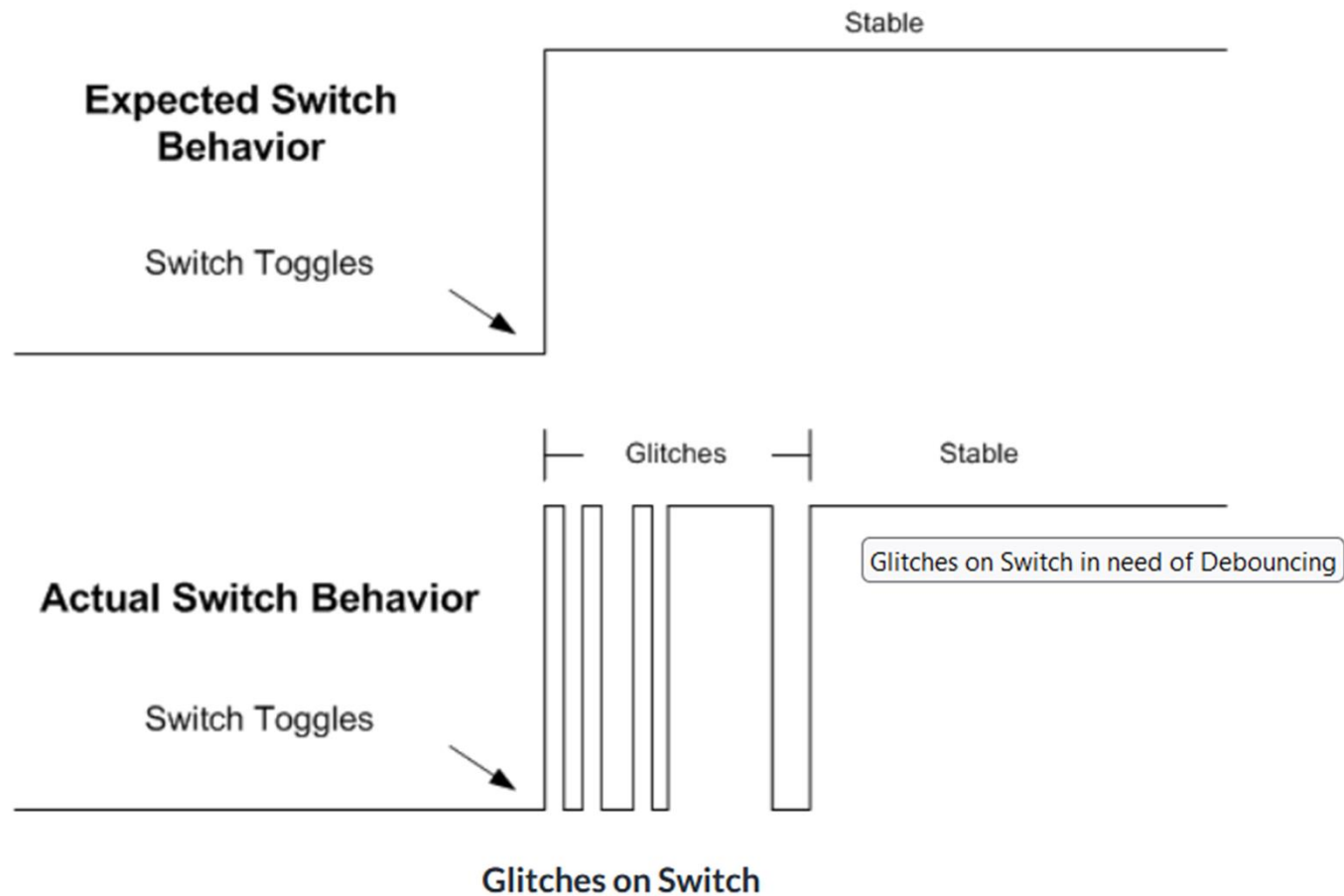


Debouncing – possible method

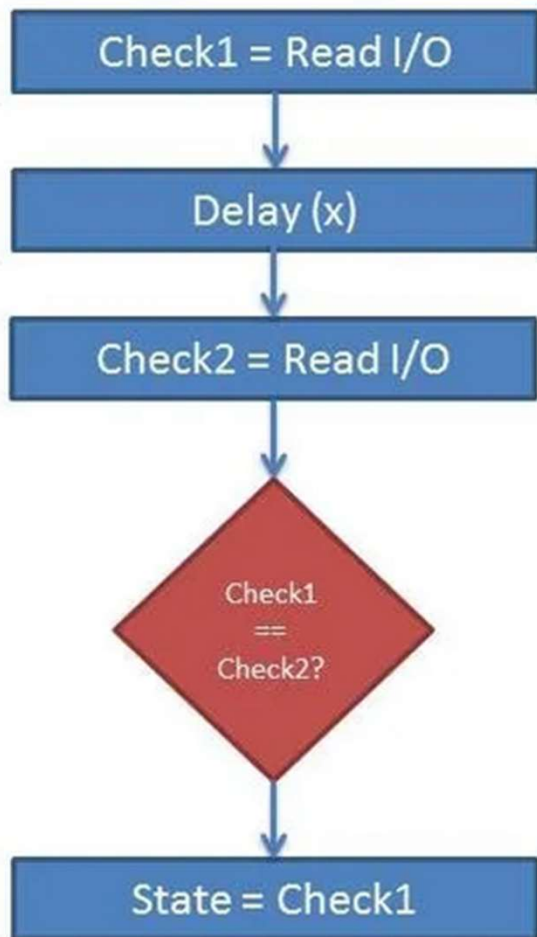

- ❑ 50 MHz clock
- ❑ 10 ms delay (worst case)
- ❑ ? Counter MAX for generating the delay ?

Clock-domain crossing (I)

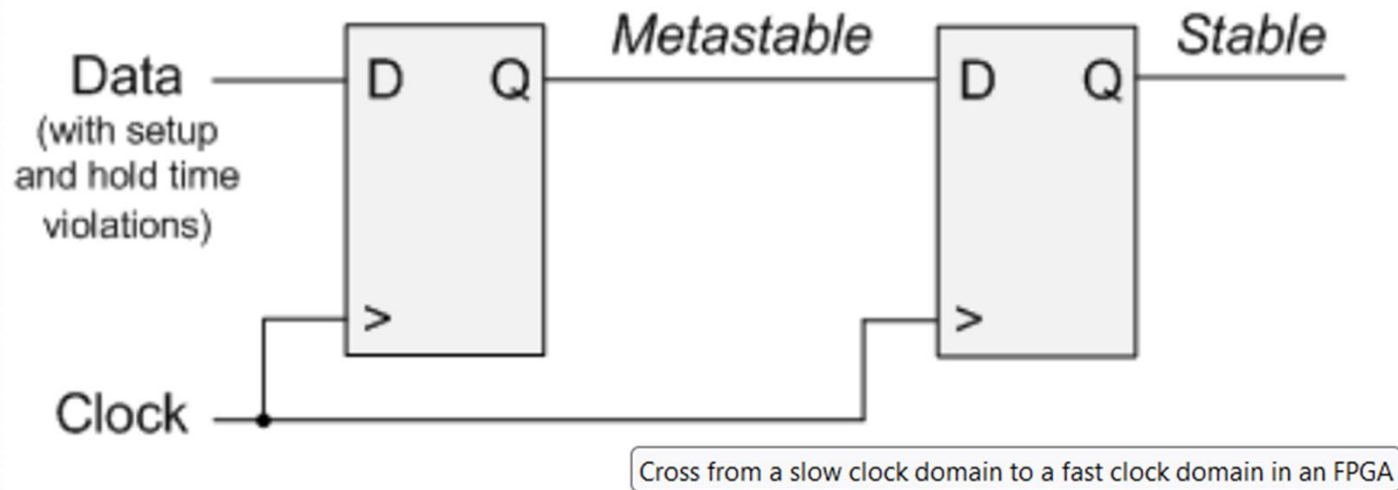❑ Crossing from slower clock domain to faster clock domain



Crossing from a slow to fast clock domain

FSM sync sw (OM) cu clock FPGA



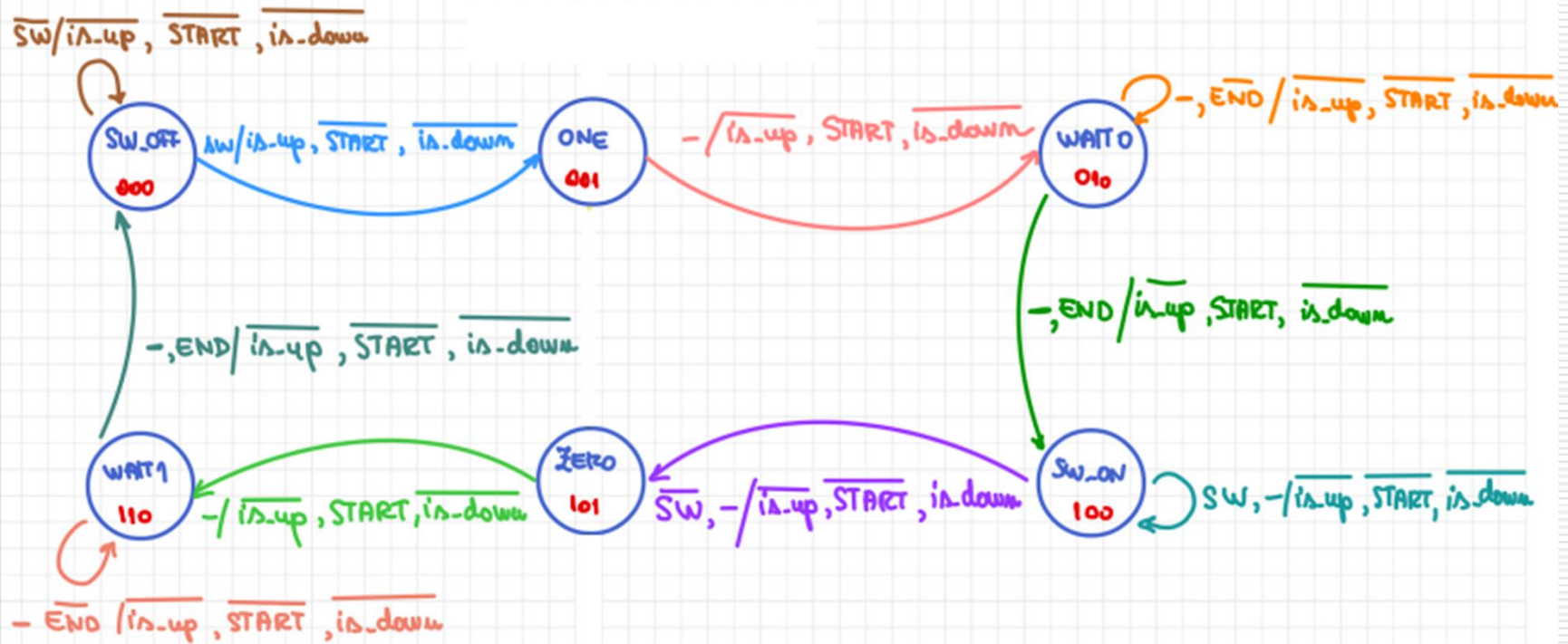


Diagrama de timp

is-up si is-down sunt edge detectors

 


Circuit

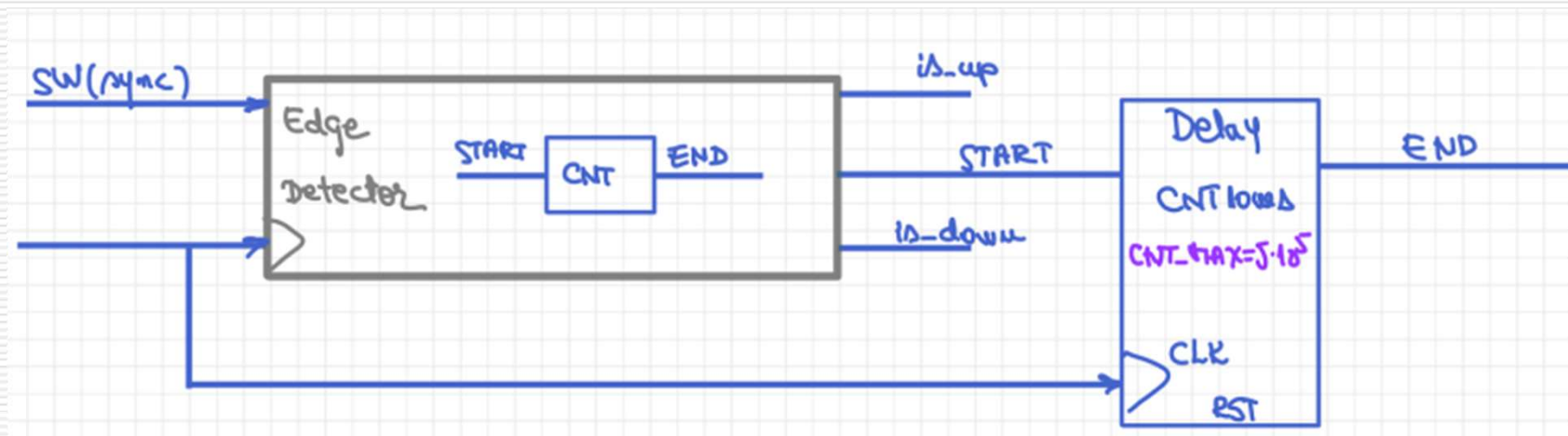

	STARE CURENTĂ			INTRĂRI		STARE URĂMĂTOARE $\equiv (n+D-w_i)$ VAL. INTRĂRI			IEȘIRI		
	Q_2	Q_1	Q_0	SW	END	$D_2(Q_2^{NXT})$	$D_1(Q_1^{NXT})$	$D_0(Q_0^{NXT})$	start	is up	is down
SW_OFF	0	0	0	0	0	0	0	0	0	0	0
				0	1	0	0	0	0	0	0
				1	0	0	0	1	0	1	0
				1	1	0	0	1			
ONE	0	0	1	*	*	0	1	0	1	0	0
WAIT0	0	1	0	*	0	0	1	0	0	0	0
				*	1	1	0	0	0	0	0
SW_ON	1	0	0	0	*	1	0	1	0	0	1
				1	*	1	0	0	0	0	0
ZERO	1	0	1	*	*	1	1	0	1	0	0
WAIT1	1	1	0	*	0	1	1	0	0	0	0
				*	1	0	0	0	0	0	0
	0	1	1	*	*	d	d	d	d	d	d
	1	1	1	*	*	d	d	d	d	d	d

Edge detector (FSM) block impl

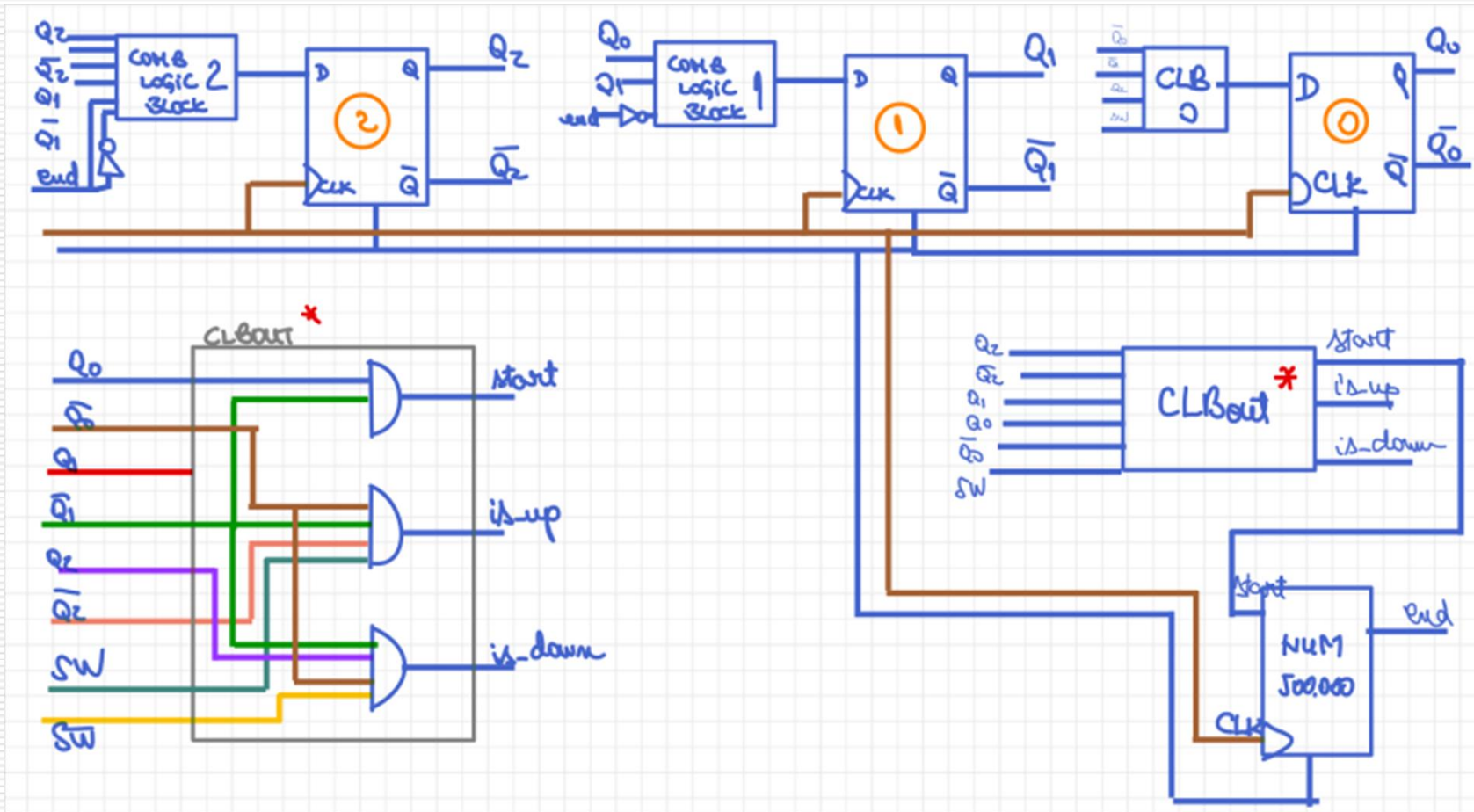

**Enough Talking Let's Get To It
!!Brace Yourselves!!**

