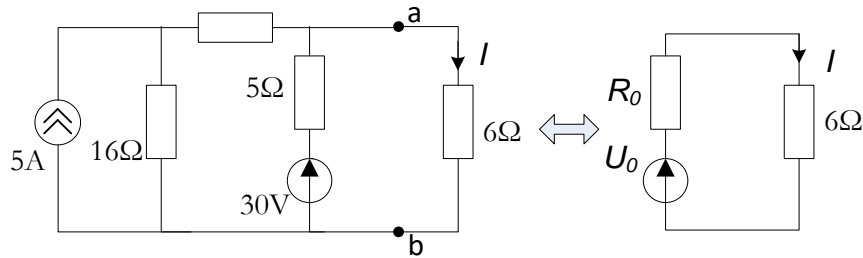


Thevenin's Theorem


Example 2.7.1. Determine the Thevenin equivalent circuit (R_0 , U_0), viewed by the 6Ω s resistance (terminals a and b) for the circuit below. Find the current I through the 6Ω s resistance.



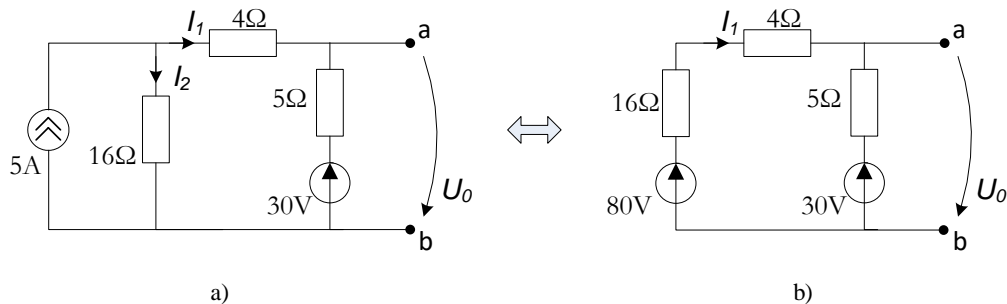
Example 2.7.1.

Solution:

The open-circuit voltage, U_0 , is the voltage between the terminals a and b by detaching the 6Ω 's resistance. For the circuit below, using KCL, we have $I_1 + I_2 = 5$, $(4 + 5) \cdot I_1 - 16 \cdot I_2 = -30$, from where solving for I_1 and I_2 , we get $I_1 = 2A$ and $I_2 = 3A$. Thus, $U_0 = 5 \cdot I_1 + 30 = 40$ (V). Another way to calculate the current I_1 is by using the source transformation theorem. The equivalent circuit is obtained in figure b), for which $(16 + 4 + 5) \cdot I_1 = 80 - 30$, and $I_1 = 2A$.



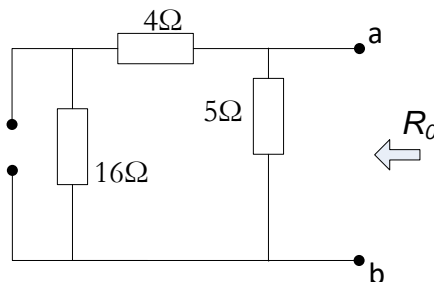To calculate the equivalent resistance R_0 of the remaining circuit, regarding the terminals a and b, we have to suppress the two sources. The passive circuit is drawn below, for which $R_0 = \frac{(16+4) \cdot 5}{16+4+5} = 4(\Omega)$.




The remaining deactivated circuit used for the calculus of the R_0

According to the Thevenin's theorem, from the equivalent circuit, the desired current is:

$$I = \frac{U_0}{R + R_0} = \frac{40}{6 + 4} = 4 \text{ (A)}.$$


Example 2.7.2. Determine the Thevenin equivalent circuit (R_0 , U_0), viewed by the 10Ω s resistance (terminals a and b) for the circuit below. Find the current I through the 10Ω s resistance.

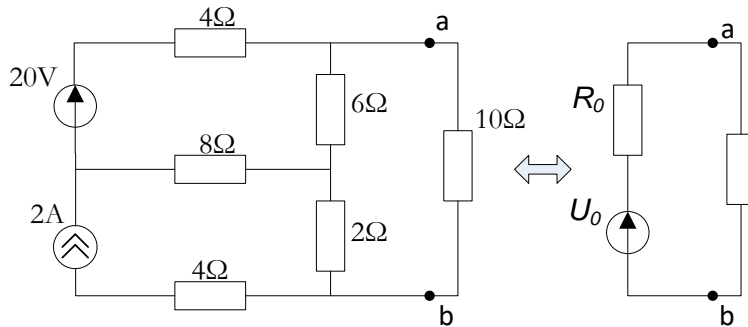

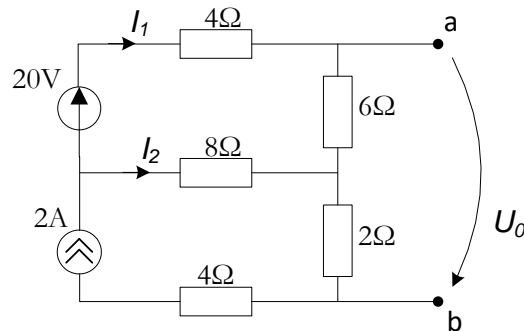Example 2.7.2.


Solution:

The open-circuit voltage, U_0 , is the voltage between the terminals a and b by detaching the 10Ω 's resistance. For the circuit below, using KCL, we have $I_1 + I_2 = 2$, $(4 + 6) \cdot I_1 - 8 \cdot I_2 = 20$, from where solving for I_1 and I_2 , we get $I_1 = 2A$ and $I_2 = 0A$. Thus, $U_0 = 6 \cdot I_1 + 2 \cdot 2 = 16 (V)$.



The remaining circuit used for the calculus of the U_0

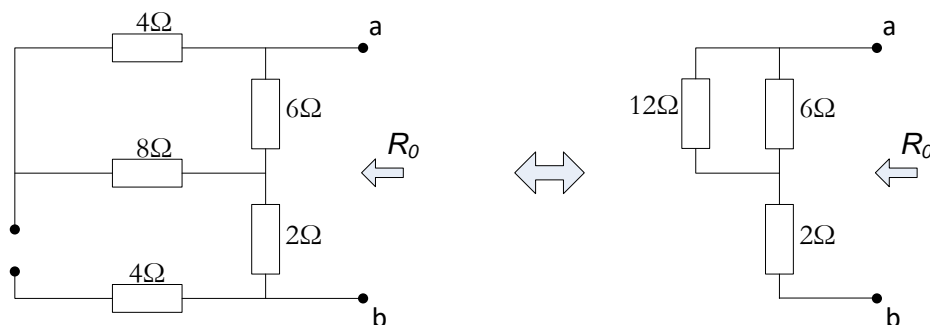To calculate the equivalent resistance R_0 of the remaining circuit, regarding the terminals a and b, we have to suppress the two sources. Figure a) shows the passive circuit which can be redrawn in an easier form in figure b). The equivalent resistance is: $R_0 = \frac{12 \cdot 5}{12 + 6} + 2 = 6(\Omega)$.



According to the Thevenin's theorem, from the equivalent circuit, the desired current is:

$$I = \frac{U_0}{R + R_0} = \frac{16}{10 + 6} = 1 (A).$$